


DEC 9, 2021

An abstract graphic on the left side of the slide. It features a wireframe globe with a network of thin black lines connecting various colored dots (yellow, blue, green, purple, cyan) scattered across its surface. The globe is partially obscured by a light gray diagonal band and a thin teal line.


# *TRANSMISSION LINES WITHOUT TEARS*

SAIED SEGHATOLESLAMI AD2CC  
GREG MAURO K3EA


# DIFFERENT ANTENNAS...

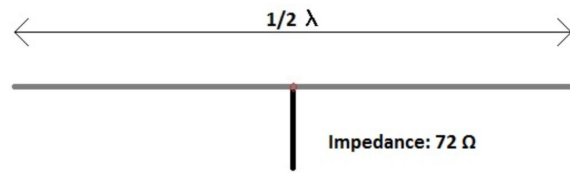


Open half wave dipole antenna

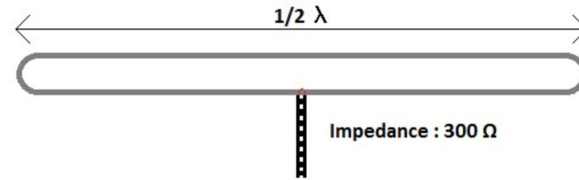


Closed half wave dipole antenna

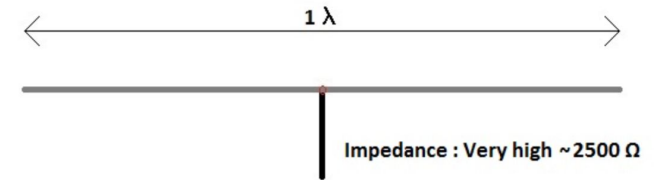


Open whole wave dipole antenna

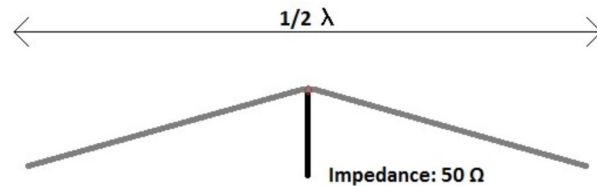



Inverted V dipole antenna

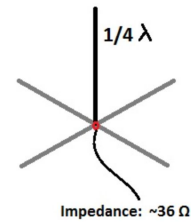


Quadrant wave vertical

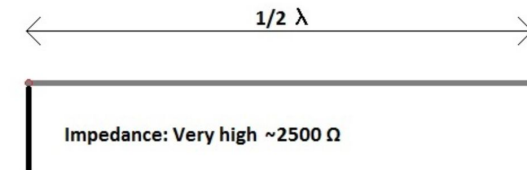

End fed half wave antenna

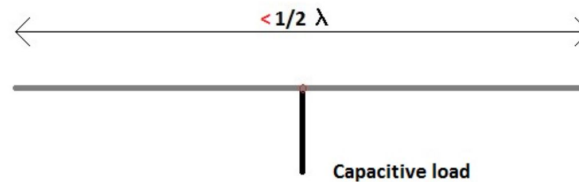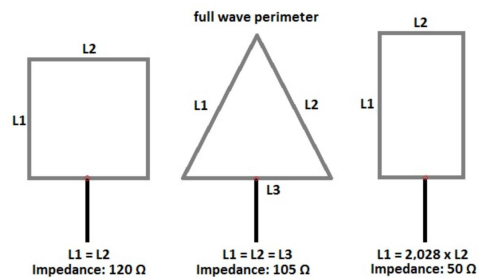

Dipole antenna too short

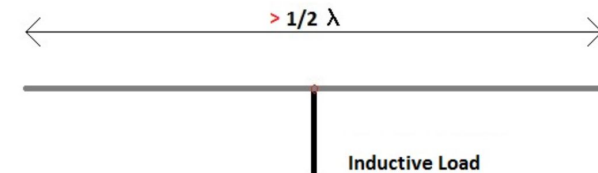

Dipole antenna too long

# *GOAL*

- Learn what makes transmission lines transmission lines
- Gain some insights into how they work
- Build efficient antenna/feedline systems
- ...with just arithmetic...
- We can do higher math at a different time

# *THINGS TO TAKE AWAY*

- A 50 Ohm coax (feedline) terminated in other than 50 ohms changes the coax impedance at its input.
- Coax (feedline) construction, material, length, and frequency all impact the above answer (your mileage will vary as you change these factors)
- The input impedance to the feedline, in most cases, will have a reactive (capacitive or inductive) component
- Power input to the feedline (into the resistive part of the input impedance) is equal to the power delivered to the load at the termination of the feedline

# *RECALL THE TECHNICIAN EXAM?*

| Question  | Answer  |
|---|---|
| How fast does a radio wave travel through free space                              | At the speed of light   |
| What is the approximate velocity of a radio wave as it travels through free space | 300,000,000 meters per second (299,792,458)                       |
| What is the name for the distance a radio wave travels during one complete cycle  | Wavelength  |
| What is the formula for converting frequency to approximate wavelength in meters  | Wavelength in meters equals 300 divided by frequency in megahertz |

One more thing: in RG8X, radio waves propagate at 79% of the speed in free space or 236,800,000 meters per second


# SO, LET'S JUST PICK A FREQUENCY

*Frequency = 14.250 MHz*

$$\text{Period} = \frac{1}{\text{Frequency}} \cong 70.18 \text{ nanoseconds}$$

Electrical wavelength in RG8X @  
14.25 MHz
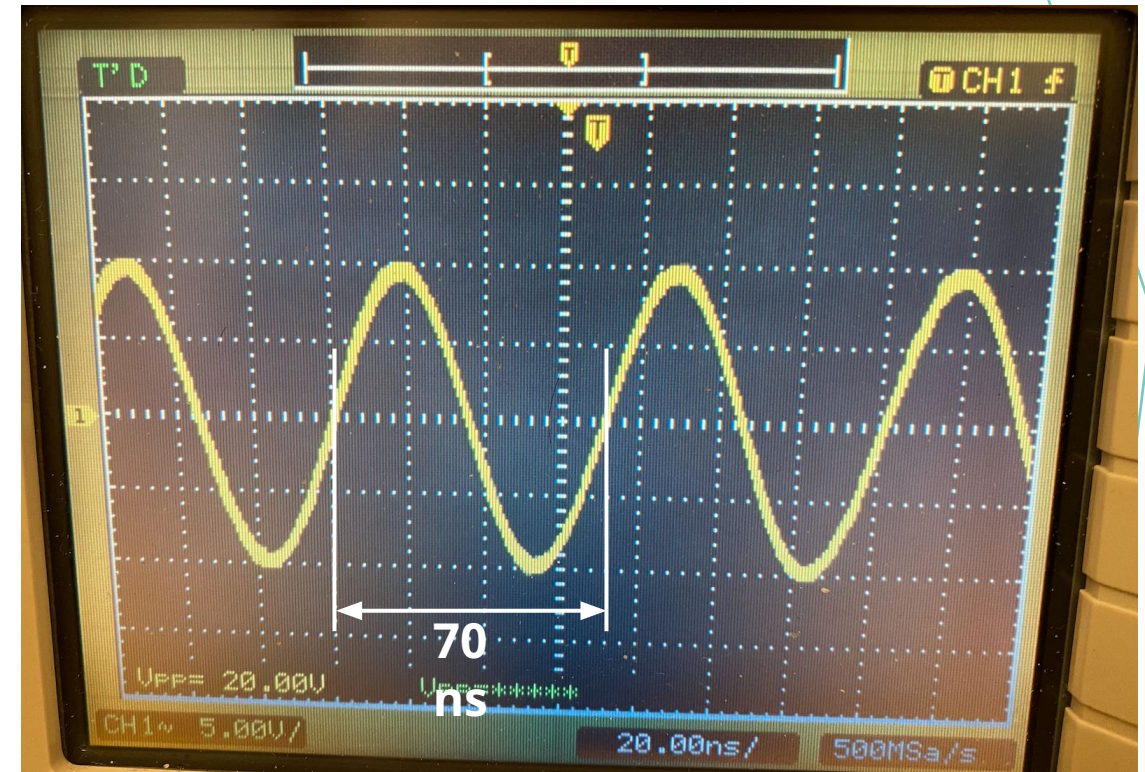
$$\text{Wavelength} = \frac{\text{Speed of propagation}}{\text{Frequency}} = \frac{237}{14.250} = 17.3 \text{ meters}$$




## *...AND A COAXIAL CABLE*

- Coax type: RG8X
- Length: 20' 7" feet = 6.3 meters
- Velocity factor: 79% (velocity in cable as a percent of velocity in vacuum)
- Impedance: 50 Ohms (resistive)
- Loss: "lossless" at HF frequencies
- Ratio of cable length to wavelength: 37%
- Cable length is an "appreciable" fraction of the wavelength



# *THE EXPERIMENTS*

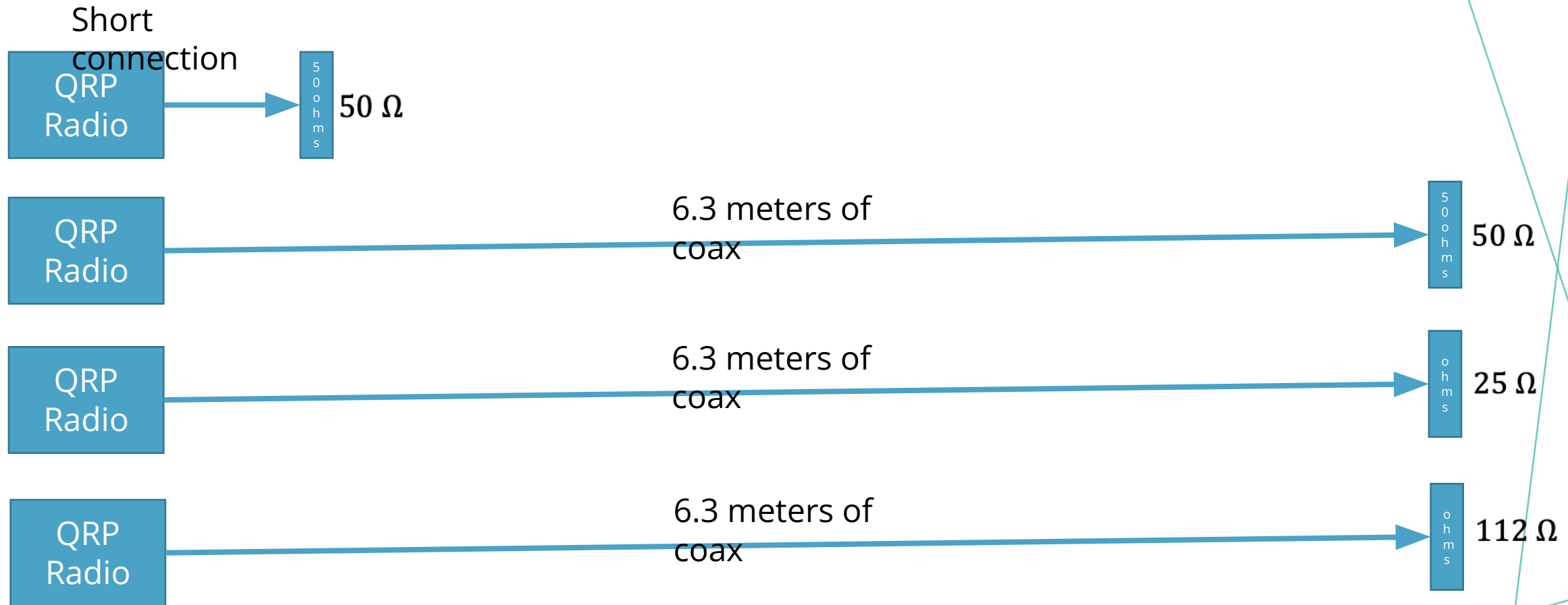



# EXPERIMENT 1 - VOLTAGE

"Short" (1.8 meter)

connection


QRP  
Radio

50 ohms

50  $\Omega$


We have already calculated period and wavelength, let's calculate the power delivered to the load.
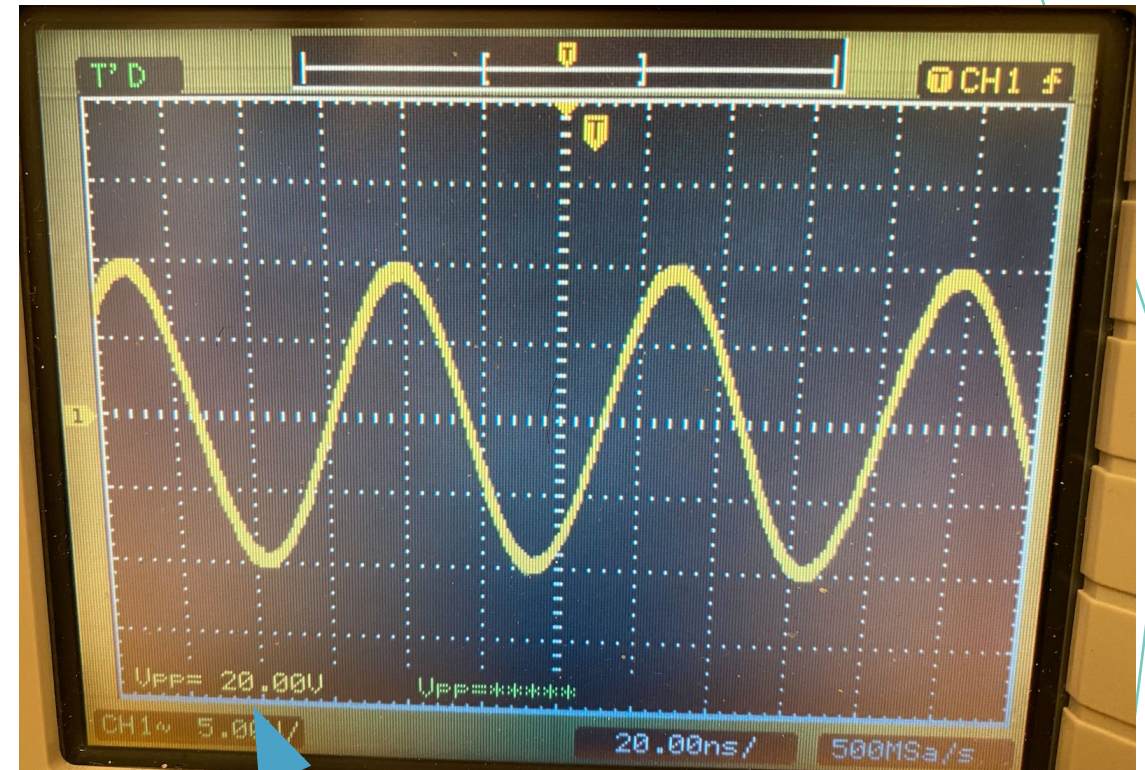
$$P_{load} = \frac{V_{rms}^2}{R_{load}} = \left( \left( \frac{20}{2} \right) \times \left( \frac{1}{\sqrt{2}} \right) \right)^2 \times \frac{1}{50} = 1.0 \text{ Watts}$$




20 Volts Peak to  
Peak

# EXPERIMENT 1 TIME

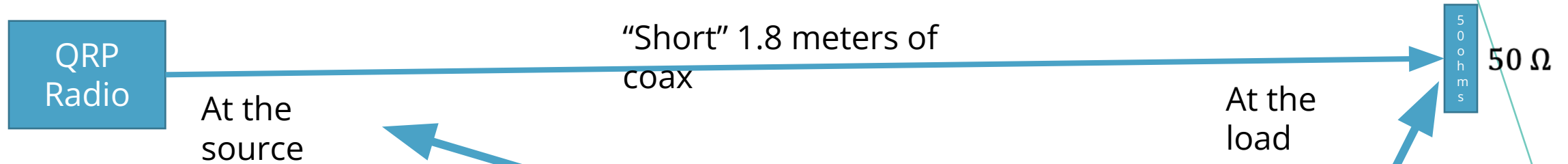

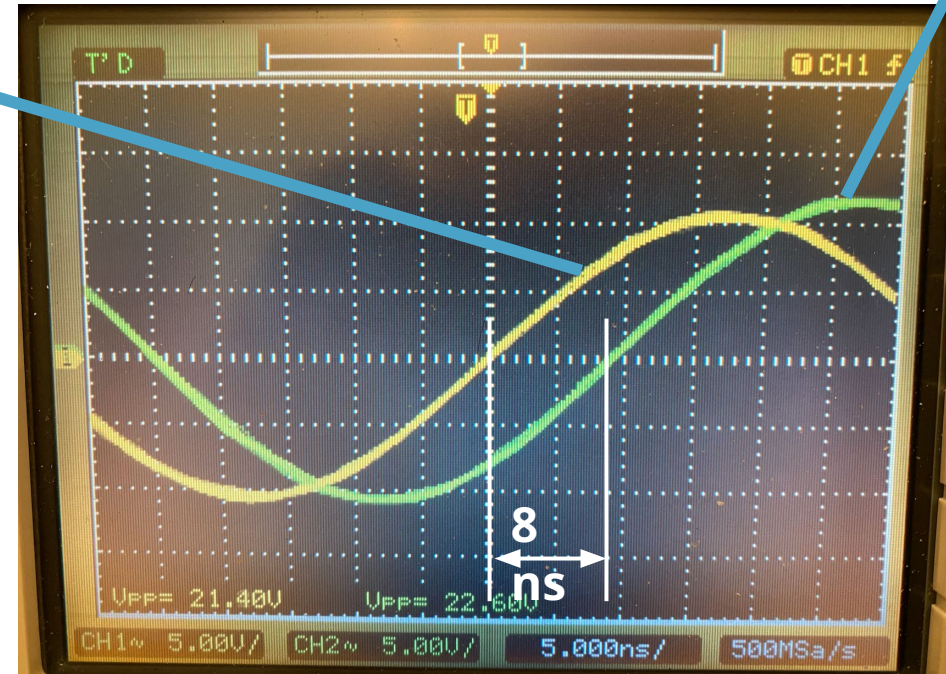
- RG8X propagation velocity:  
236,800,000 m/s
- $1.8 \text{ m} / 236,800,000 \text{ m/s} = 7.6 \text{ ns}$



**Voltage is delayed about 8 ns at the load from the source**




# SIDETRACK: MEASURING CURRENT

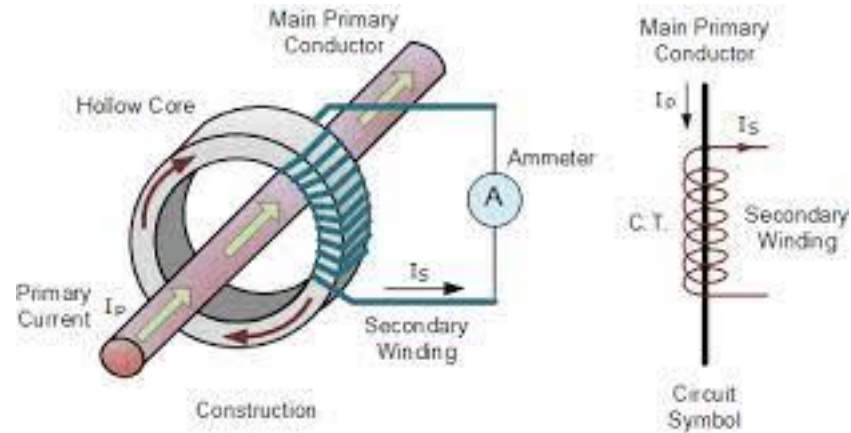

Shield  
d

100  
Ohms

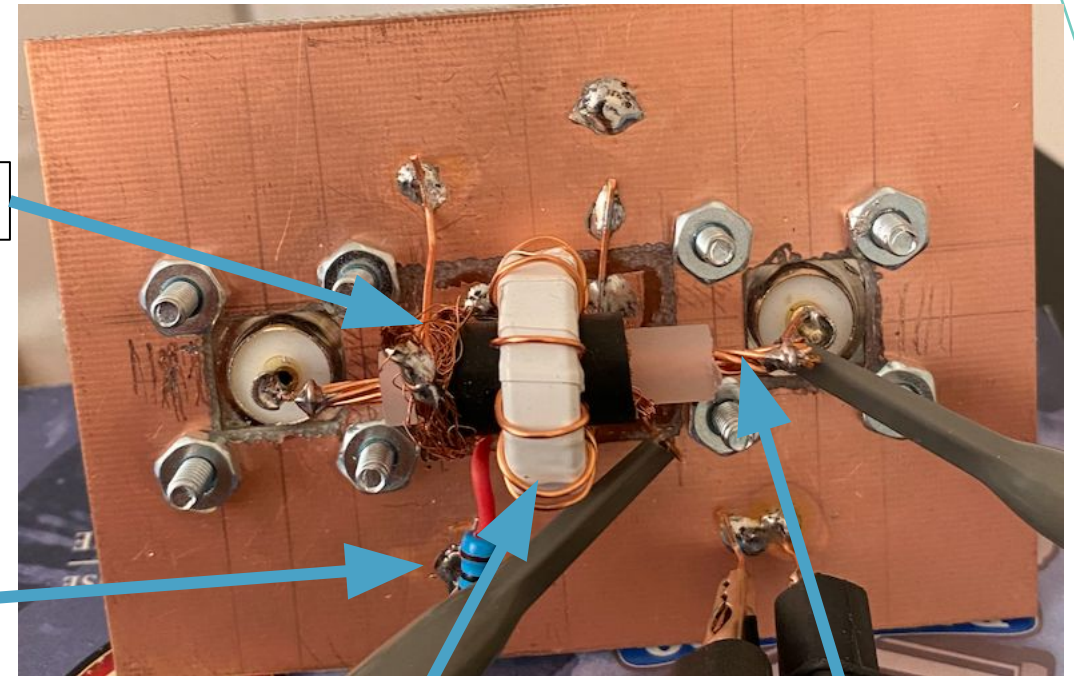


11 turn  
secondary


1 turn  
primary  
(coax  
cable)

Instead of measuring current in the secondary, we put 100 ohms across the secondary and measure voltage

# EXPERIMENT 1 – CURRENT

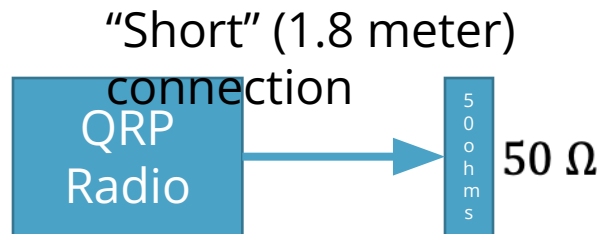

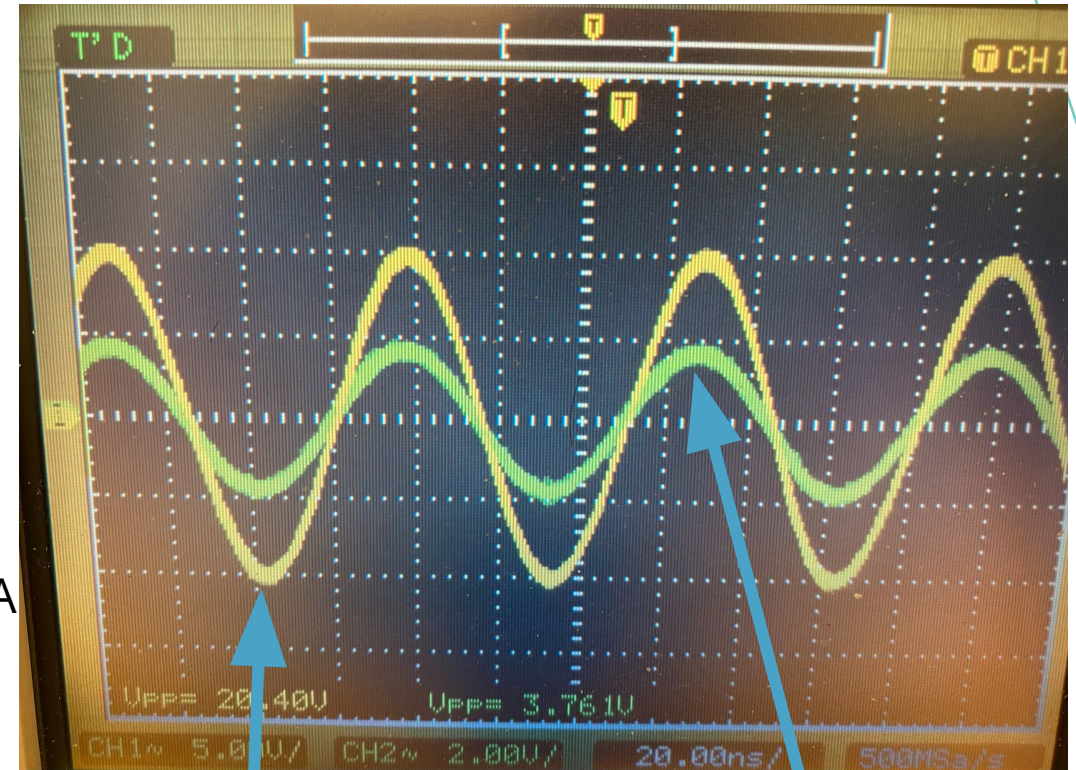- Note: current is in phase with voltage indicating resistive load
  - 3.76 volts peak to peak / 2 = 1.88 volts peak
  - 1.88 volts / 100 ohms = 18.8 mA peak
  - 18.8 mA peak (secondary) x 11 turns ratio = 206.8 mA peak (primary)
  - 206.8 mA / 1000 = 0.2068 A peak in primary
- $$P_{load} = (I_{rms})^2 R_{load} = \left(0.2068 \frac{\text{A}}{\sqrt{2}}\right)^2 \times 50 = 1.07 \text{ Watts}$$




Voltage

Secondary voltage  
(current)


Using the voltage or the current formula for power, we get the same



# EXPERIMENT 2 - VOLTAGE

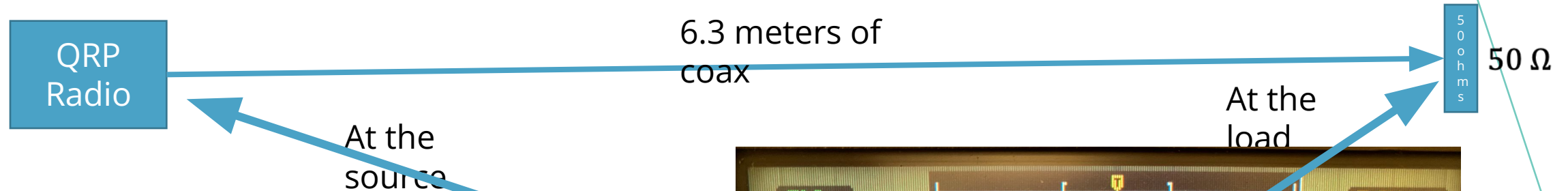


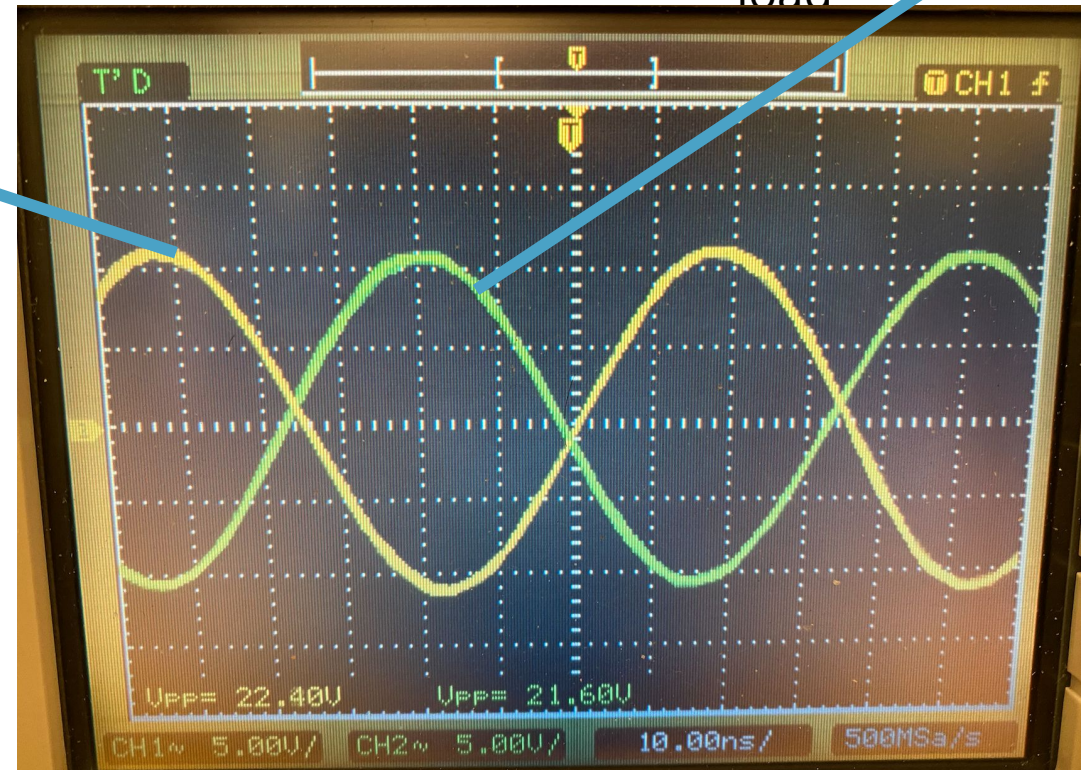- ~1 Watt into the cable
- ~1 Watt delivered to the load




**There is a delay between voltage at the load and the source**

# EXPERIMENT 2 TIME

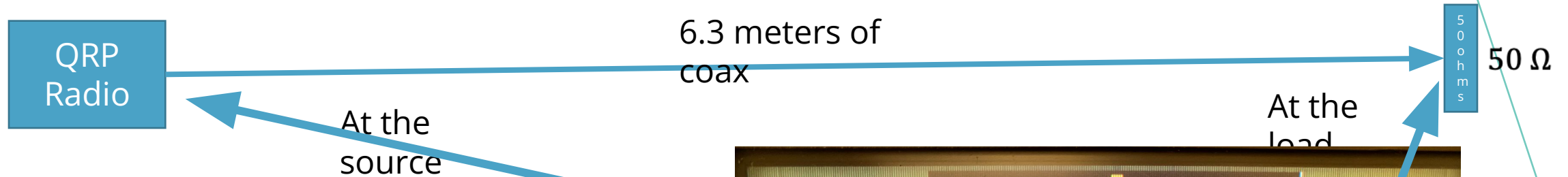

$$\frac{6.3 \text{ meters}}{236.8 \text{ million m/s}} = 26.6 \text{ nano seconds}$$

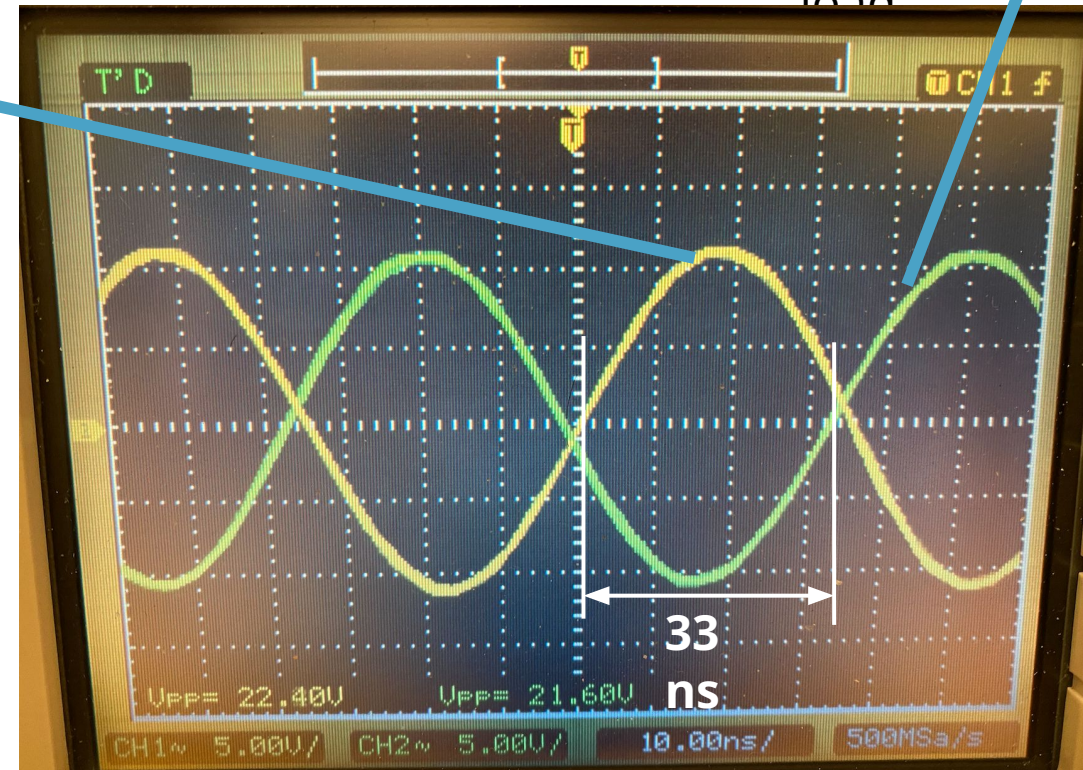- What causes the difference?
- Stray inductance and capacitance?
- Measurement error?
- The RG8X used has a velocity of 191 million miles per second
- ...or a little bit of all the above...



**There is a delay 33 ns between voltage at the load and the source**




# EXPERIMENT 2 CURRENT

QRP  
Radio

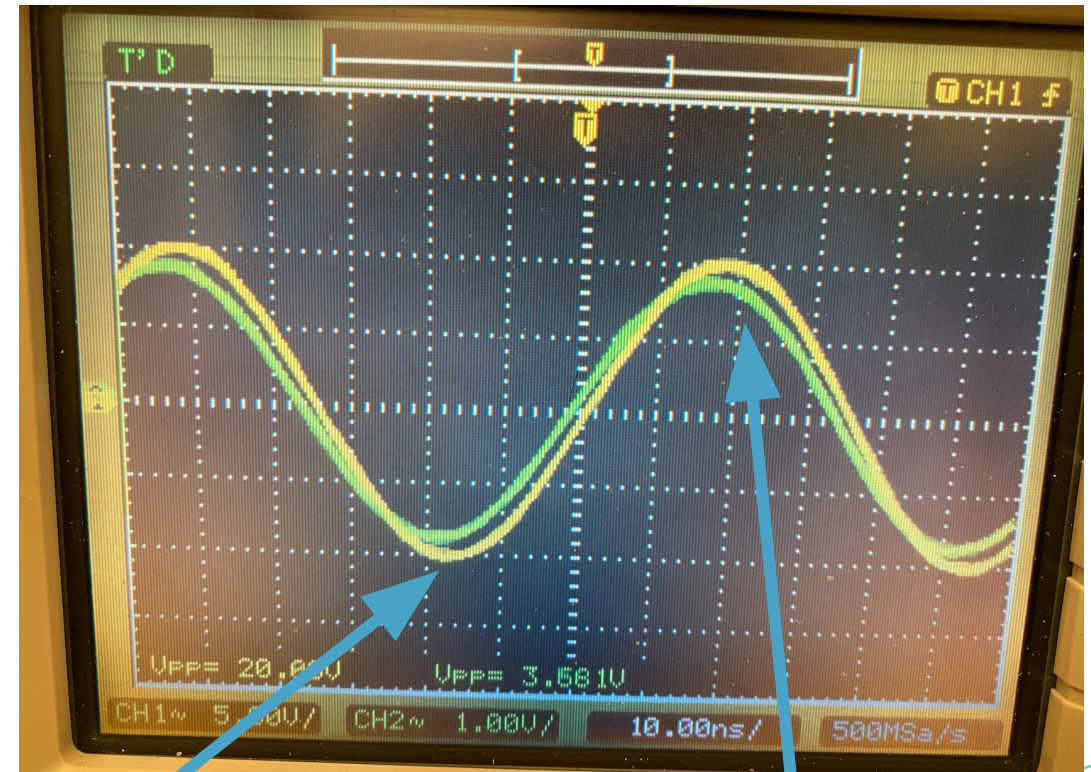6.3 meters of  
coax

ohms  
50  $\Omega$

- Note: current is in phase with voltage indicating resistive load
  - 3.68 volts peak to peak / 2 = 1.84 volts peak
  - 1.88 volts / 100 ohms = 18.4 mA peak
  - 18.4 mA peak in secondary x 11 = 202.4 mA peak in primary
  - 202.4 mA / 1000 = 0.2024 A peak in primary
- $$P_{load} = (I_{rms})^2 R_{load} = \left(0.2024 \frac{1}{\sqrt{2}}\right)^2 \times 50 = 1.02 \text{ Watts}$$




Volta  
ge

Secondary voltage  
(current)



# EXPERIMENT 3 VOLTAGE

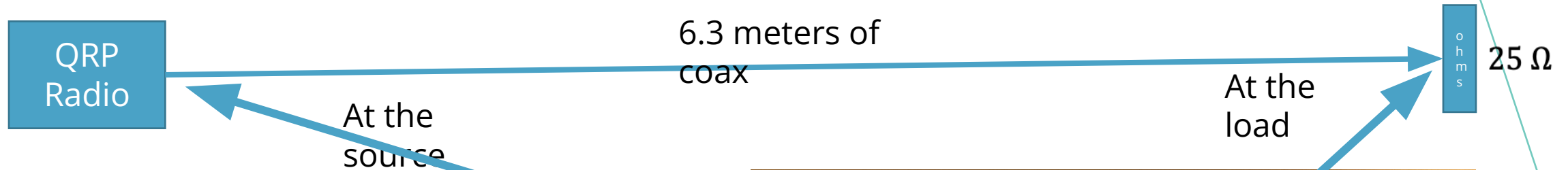


What happened, where does 14.00 volts and 12.16 volts come from?

Power delivered to the load (remember this number):


$$P_{load} = \frac{V_{rms}^2}{R_{load}} = \left( \frac{12.16}{2} \times \frac{1}{\sqrt{2}} \right)^2 \times \frac{1}{25} = 744 \text{ mW}$$



# EXPERIMENT 3 VOLTAGE

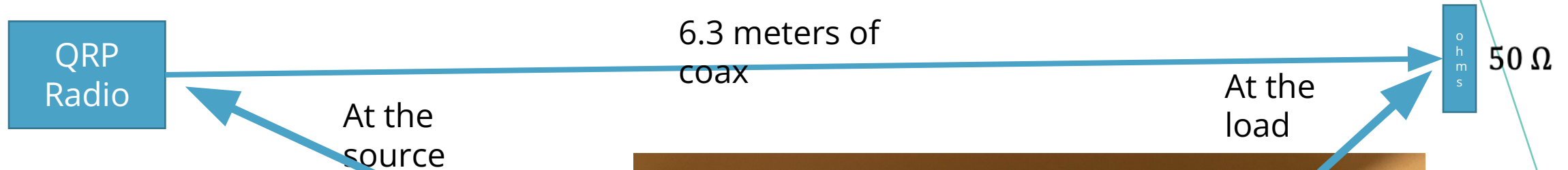


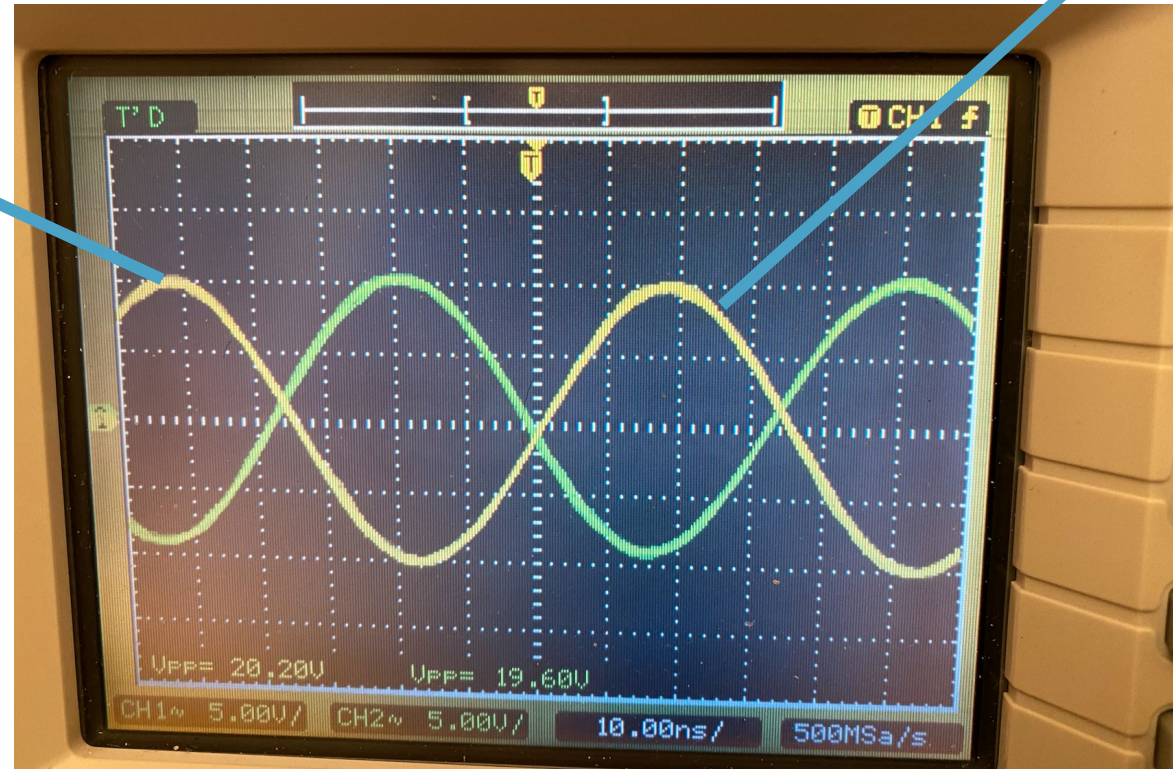Insight  
Terminating a transmission  
line with other than its  
characteristic impedance






# EXPERIMENT 3 CURRENT

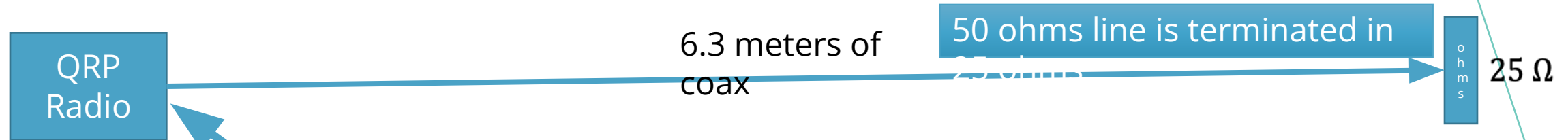
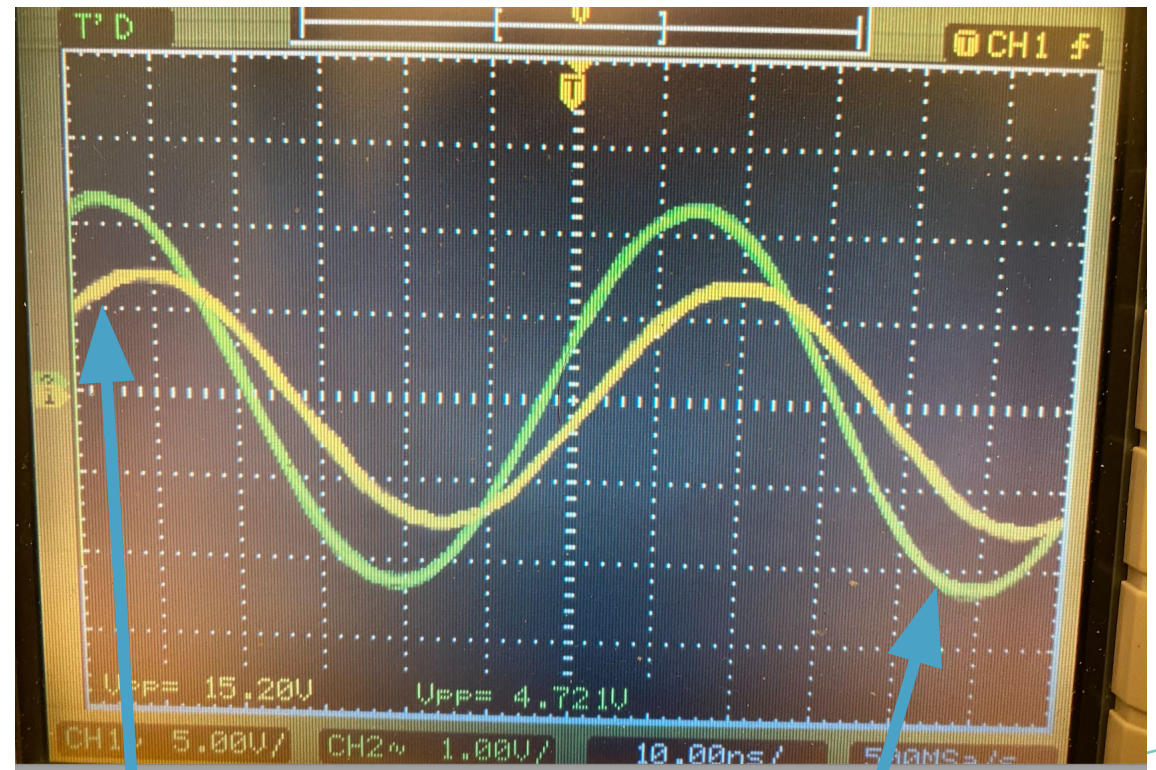
## At the input to the line:

- Current leads voltage by 7 ns (10% of period)
- Load has a capacitive component
- ELI the ICE man
  - Voltage leads current in an inductor
  - Current leads voltage in a capacitor



Voltage


Secondary voltage  
(current)

# *EXPERIMENT 3 THE MATH*

- Voltage at the input 15.2 volts peak to peak
- Voltage across the current sensing resistor 4.72 volts peak to peak
- $4.72 / 100 = 47.2$  mA peak to peak
- $47.2 \text{ mA} \times 11 = 519.2$  mA peak to peak
- $519.2 \text{ mA} / 1000 = 0.5192$  A
- $15.2 \text{ volts} / 0.5192 \text{ A} = 29.3$  Ohms (23.7 ohms resistive and 17.2 ohms capacitive)

$$P = \left( \frac{0.5192}{2} \times \frac{1}{\sqrt{2}} \right)^2 \times 23.7 = 0.788 \text{ W} = 798 \text{ mW}$$


# EXPERIMENT 4 VOLTAGE

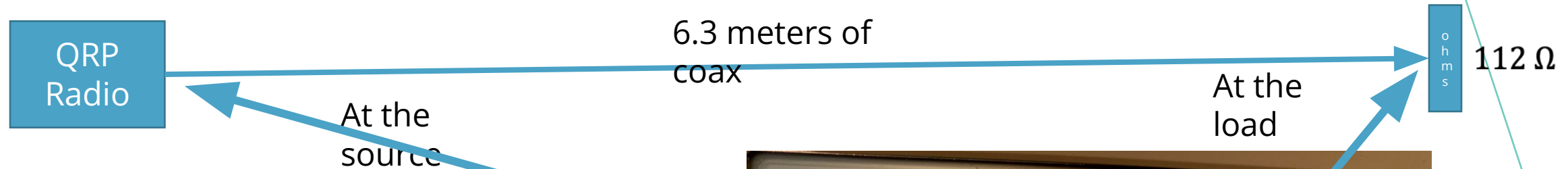

...the same story, the 28 volts and 29.6 volts are related to the 20 volts with a 50 ohm load the same way as the 14.00 volts and 12.16 volts form the 25 ohms case?

Power delivered to the load (remember this number):
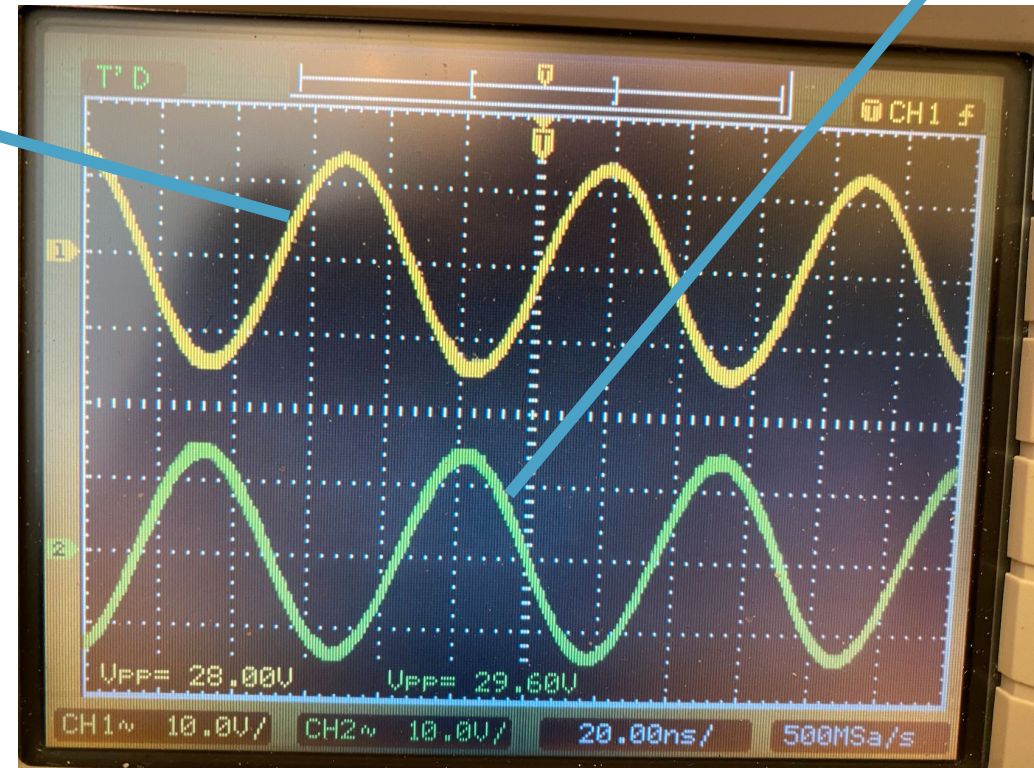
$$P_{load} = \frac{V_{rms}^2}{R_{load}} = \left( \frac{29.6}{2} \times \frac{1}{\sqrt{2}} \right)^2 \times \frac{1}{112} = 978 \text{ mW}$$





# EXPERIMENT 4 CURRENT


QRP  
Radio

6.3 meters of  
coax

50 ohms line is terminated in


ohms

112  $\Omega$

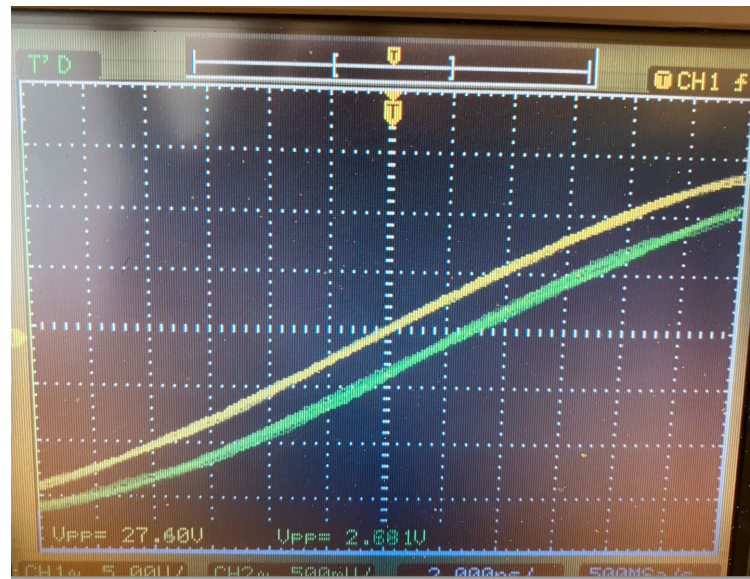
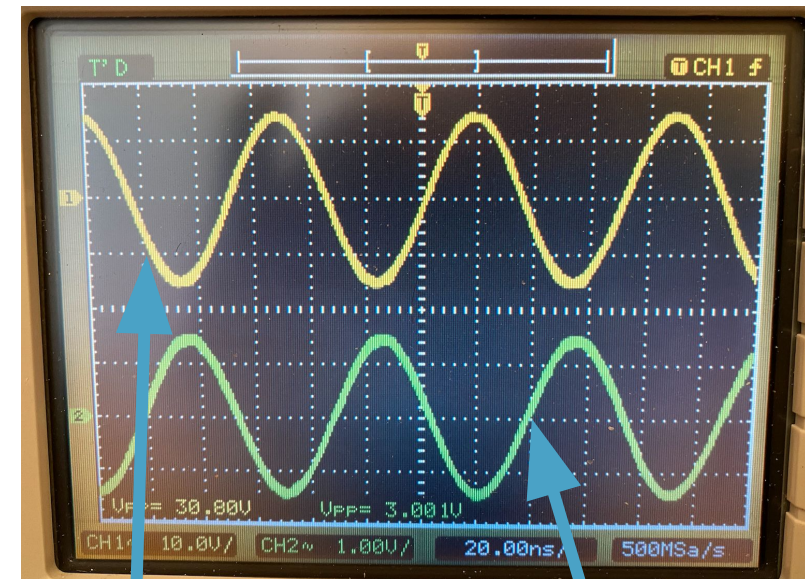
## At the input to the line:

- Voltage leads current by 3 ns (4.3% of period)
- Load has an inductive component
- Fill the ICE map



Voltage

Secondary voltage  
(current)

# *EXPERIMENT 4 THE MATH*

- Voltage at the input 27.7 volts peak to peak
- Voltage across the current sensing resistor 2.68 volts peak to peak
- $2.68 / 100 = 26.8$  mA peak to peak
- $26.8 \text{ mA} \times 11 = 294.8$  mA peak to peak
- $294.8 \text{ mA} / 1000 = 0.2948$  A peak to peak
- $27.7 \text{ volts} / 0.2948 \text{ A} = 94.0$  Ohms (90.6 ohms resistive and 24,9 ohms inductive)

$$P = (I_{rms})^2 R = \left( \frac{0.2948}{2} \times \frac{1}{\sqrt{2}} \right)^2 \times 90.6 = 0.956 \text{ W} = 984 \text{ mW}$$




# *INSIGHTS*

- This data is for one length of cable, one frequency, and three terminations
- Other situations will give different results, but it gives you an idea what is at work
- Terminating a line in its characteristic impedance makes it appear as if it is not there (except for the wave travel time)
- Terminating a line in a different impedance changes the input impedance of the line (and often with a reactive, capacitance or inductance, component)
- The change depends on the cable, the frequency, the length and the termination

Power delivered to the input is always equal to the power

# *WHAT DO YOU DO, PRACTICALLY*

- Your radio is designed for best performance with 50 Ohms load
- ...but who has a pure 50 ohms resistive antenna?
- Build or buy as good an antenna as you can (consult Greg)
- Your feedline impedance is most likely 50 ohms
- So, your radio will see a different impedance and that depends...
- At an SWR of 2, you will lose 10% of your power output and at an SWR of 3, about 25% of power, so keep your SWR close to 2 or less...

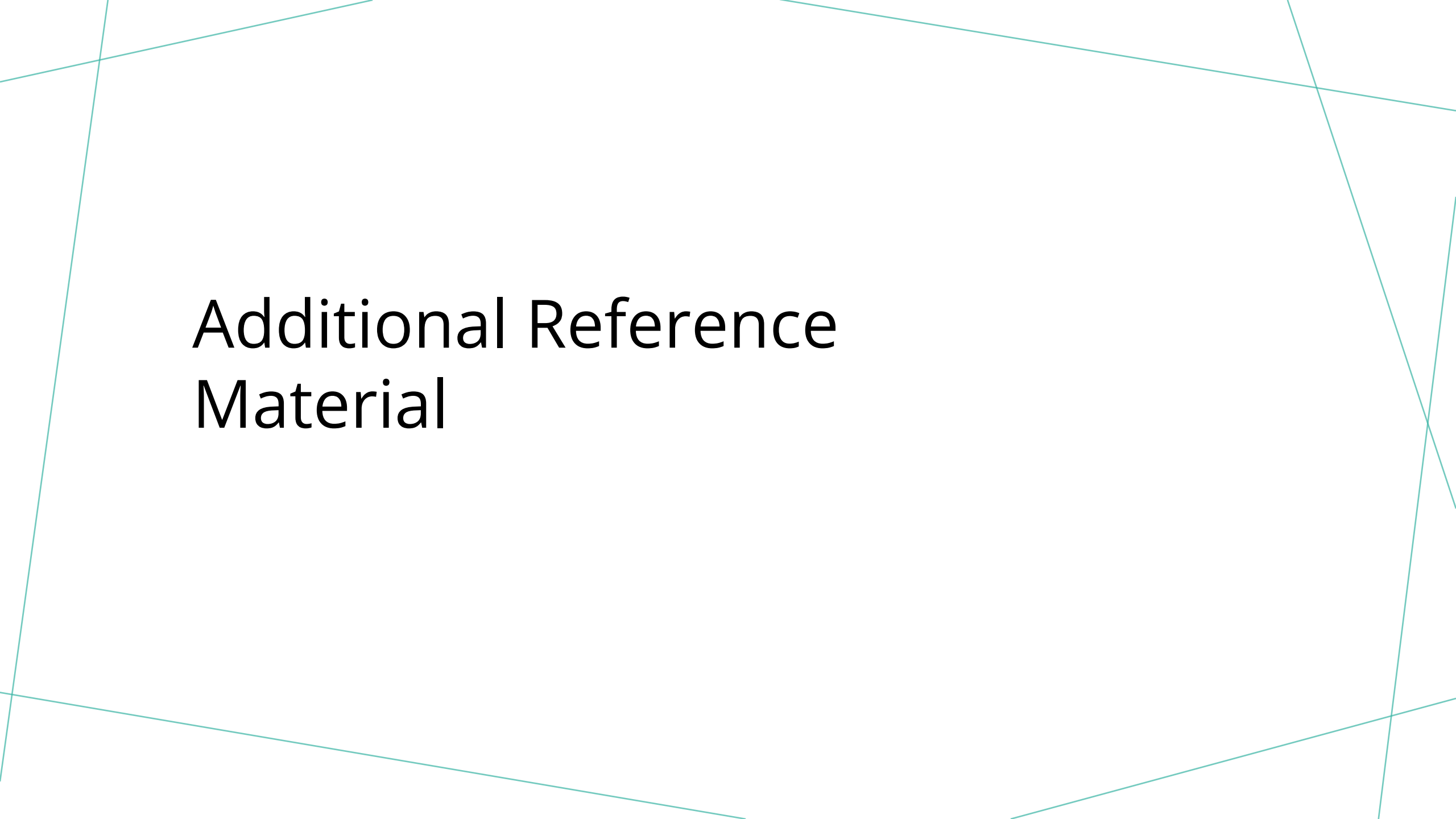The background features several thin, teal-colored lines that intersect to form a series of irregular, overlapping polygons. These lines are positioned primarily around the edges of the frame, creating a modern, geometric aesthetic.

# Additional Reference Material

# REFLECTION

- When a wave (of any kind) hits a mismatch in its traveling medium, some of the wave will reflect back
- As we have seen, when the line is terminated with a matching impedance, the full power of the wave is delivered to the load and that is the end of the story
- ...But what if it is not? Let's dig into that.

$$\text{reflection coefficient} = \frac{\text{reflected voltage}}{\text{forward voltage}} = \frac{\text{load impedance} - \text{line impedance}}{\text{load impedance} + \text{line impedance}}$$

$$\text{reflection coefficient(at } 25\Omega) = \frac{\text{reflected voltage}}{\text{forward voltage}} = \frac{25 - 50}{25 + 50} = -.333$$

$$\text{reflection coefficient(at } 112\Omega) = \frac{\text{reflected voltage}}{\text{forward voltage}} = \frac{112 - 50}{112 + 50} = .383$$

# REFLECTION

$$\text{reflection coefficient} = \frac{\text{reflected voltage}}{\text{forward voltage}} = \frac{\text{load impedance} - \text{line impedance}}{\text{load impedance} + \text{line impedance}}$$

$$\text{reflection coefficient} = \frac{\text{reflected voltage}}{\text{forward voltage}} = \frac{25 - 50}{25 + 50} = -0.333$$

$$\text{reflected voltage} = -0.333 \times \text{forward voltage}$$

$$\text{load voltage} = \text{forward voltage} + \text{reflected voltage} = 12.16 \text{ volts}$$

$$\text{forward voltage} = 18.23 \text{ volts}$$

$$\text{reflected voltage} = -6.1 \text{ volts (} - \text{sign indicates 180 degree phase shift)}$$

And just for  
reference:

$$SWR(at\ 25\Omega) = \frac{1 + \text{absolute value of reflection coefficient}}{1 - \text{absolute value of reflection coefficient}} = \frac{1 + .333}{1 - .333} = 2$$

$$SWR(at\ 112\Omega) = \frac{1 + .383}{1 - .383} = 2.2$$

$$\text{absolute value of reflection coefficient} = \frac{SWR - 1}{SWR + 1}$$